

Circuits and Transforms

Gautam Singh

CONTENTS

1 Bilinear Transform 1

Abstract—This manual provides a simple introduction to Transforms

1 BILINEAR TRANSFORM

1. Formulate the differential equation for Fig. 1.1.

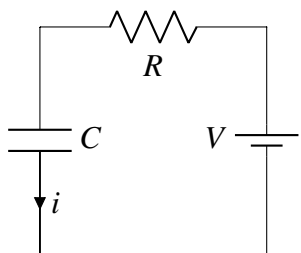


Fig. 1.1

Solution: Applying KVL on the loop,

$$V - iR - \frac{1}{C} \int_0^t i dt = 0 \quad (1.1)$$

where $i(0) = 0$, $V_C(0) = 0$. Denote by V_C the voltage at the capacitor. Then,

$$i = C \frac{dV_C}{dt} \quad (1.2)$$

and therefore using (1.2) in (1.1), we get the differential equation

$$V - \tau \frac{dV_C}{dt} - V_C = 0 \quad (1.3)$$

where $\tau \triangleq RC$ is the time constant of the circuit.

2. Find $H(s)$ considering the output voltage at the capacitor.

Solution: Transforming Fig. 1.1 to the s -domain,

Thus, using the voltage division formula, the voltage across the capacitor is given by

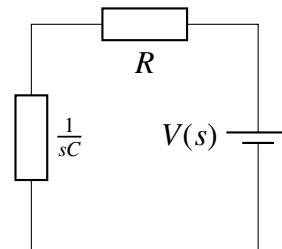


Fig. 1.2

$$V_C(s) = V(s) \frac{\frac{1}{sC}}{\frac{1}{sC} + R} \quad (1.4)$$

$$= V(s) \frac{1}{1 + sCR} \quad (1.5)$$

Therefore, the transfer function is given by

$$H(s) = \frac{V_C(s)}{V(s)} = \frac{1}{1 + sCR} \quad (1.6)$$

3. Plot $H(s)$. What kind of filter is it?

Solution: The Python code `codes/1_3.py` plots $H(s)$. Clearly, $H(s)$ is a low-pass filter.

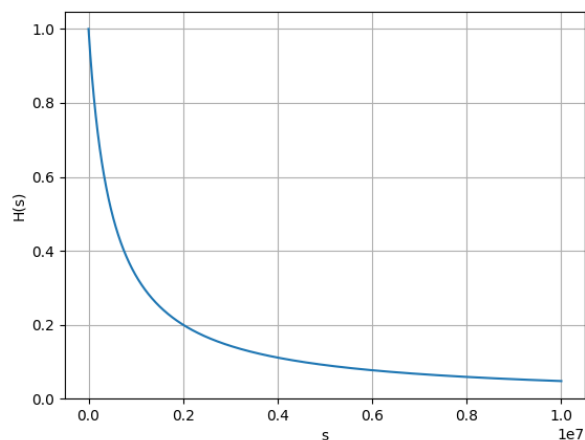


Fig. 1.3: Plot of $H(s)$.

4. Using trapezoidal rule for integration, formu-

late the difference equation by considering

$$y(n) = y(t)|_{t=n} \quad (1.7)$$

Solution: Integrating (1.3) between limits $n-1$ to n and applying the trapezoidal formula,

$$\begin{aligned} \frac{v_C(n) + v_C(n-1)}{2} + \tau(v_C(n) - v_C(n-1)) \\ = \frac{V(n) + V(n-1)}{2} \end{aligned} \quad (1.8)$$

for $n > 0$, where $v(0) = 0$.

5. Find $H(z)$.

Solution: Applying the Z-transform on both sides of (1.8),

$$V_C(z) \left[(2\tau + 1) - z^{-1}(2\tau - 1) \right] = V(z) (1 + z^{-1}) \quad (1.9)$$

Hence,

$$H(z) = \frac{1 + z^{-1}}{(2\tau + 1) - (2\tau - 1)z^{-1}} \quad (1.10)$$

since $\left| \frac{2\tau-1}{2\tau+1} \right| < 1$, the ROC is $|z| > 1$.

6. How can you obtain $H(z)$ from $H(s)$?

Solution: We use the bilinear transformation. Setting

$$s \triangleq \frac{2}{T} \frac{1 - z^{-1}}{1 + z^{-1}} \quad (1.11)$$

we get

$$H(z) = \frac{1}{1 + \frac{2\tau}{T} \frac{1 - z^{-1}}{1 + z^{-1}}} \quad (1.12)$$

Setting $T = 1$ gives (1.10).

7. Find $v_C(n)$. Verify using ngspice and the differential equation.

Solution: Note that $v(n) = V u(n)$. Thus,

$$V(z) = \frac{V}{1 - z^{-1}} \quad (1.13)$$

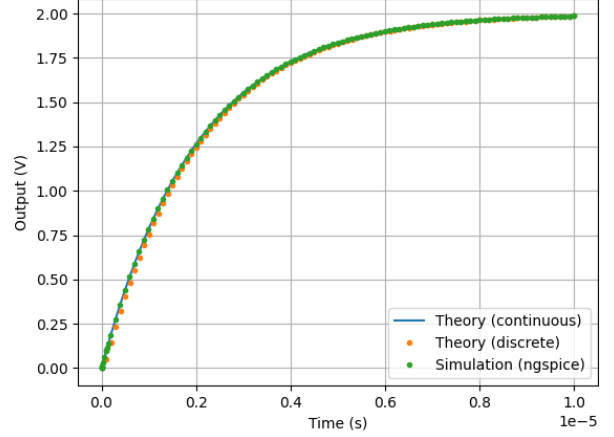


Fig. 1.7: Representation of output across C .

Therefore,

$$V_C(z) = H(z)V(z) \quad (1.14)$$

$$\begin{aligned} &= \frac{TV(1 + z^{-1})}{(1 - z^{-1})((2\tau + T) - (2\tau - T)z^{-1})} \end{aligned} \quad (1.15)$$

$$= \frac{V(1 + z^{-1})}{2} \sum_{k=-\infty}^{\infty} (1 - p^k) u(k) z^{-k} \quad (1.16)$$

where $p \triangleq \frac{2\tau-T}{2\tau+T}$. Thus,

$$v_C(n) = \begin{cases} \frac{V}{2} [u(n)(1 - p^n) + u(n-1)(1 - p^{n-1})] & n > 0 \\ 0 & n \leq 0 \end{cases} \quad (1.17)$$

We take $T = 10^{-7}$ as the sampling interval. The python code `codes/1_7.py` verifies these equalities.